

Worksheet M5

rev. 1

1. Resistance measurement using the LCR - meter

$R_1 = \dots\dots\dots$ $\Delta R_1 = \dots\dots\dots$ $\epsilon_{R1} [\%] = \dots\dots\dots$
 $R_2 = \dots\dots\dots$ $\Delta R_2 = \dots\dots\dots$ $\epsilon_{R2} [\%] = \dots\dots\dots$
 $R_3 = \dots\dots\dots$ $\Delta R_3 = \dots\dots\dots$ $\epsilon_{R3} [\%] = \dots\dots\dots$

2. Using the sort method for determining the tolerance of a resistance

$\Delta R_1 [\%] = \dots\dots\dots$ $\Delta R_2 [\%] = \dots\dots\dots$ $\Delta R_3 [\%] = \dots\dots\dots$

3. Measurement of small resistances

$R_{\text{quadri}} = \dots\dots\dots$ b) $R_{\text{bipolar}} = \dots\dots\dots$
c) $R_{\text{contact wire}} = \dots\dots\dots$ $\Delta R = \dots\dots\dots$
d) $R_{\text{corrected}} = \dots\dots\dots$ $\epsilon_R [\%] = |R_{\text{quadri}} - R_{\text{corrected}}| / R_{\text{quadri}} = \dots\dots\dots$

Explanation:

e) $R_{\text{wire quadri}} = \dots\dots\dots$ b) $R_{\text{wire bipolar}} = \dots\dots\dots$

4. Measurement of capacitors and inductors

a) $C_{s1} = \dots\dots\dots$ $D_1 = \dots\dots\dots$ $Q_1 = 1/D = \dots\dots\dots$ $C_{p1} = \dots\dots\dots$
 $C_{s2} = \dots\dots\dots$ $D_2 = \dots\dots\dots$ $Q_2 = 1/D = \dots\dots\dots$ $C_{p2} = \dots\dots\dots$

*Explanation:**How is the quality factor of capacitors ?**How are the values of C_s and C_p ? Why?*

b) $L_s = \dots\dots\dots$ $Q = \dots\dots\dots$ $L_p = \dots\dots\dots$ $R_s = \dots\dots\dots$ $Q_{\text{Calc}} = \dots\dots\dots$

Observations:

f(kHz)	10	33	66	100
L (measured)				

Explanation: What happens to the inductance value? Why?

5. Measuring the RC circuit

$f=1kHz:$

$C_s = \dots\dots\dots$ $C_p = \dots\dots\dots$
 $D = \dots\dots\dots$ $Q = 1/D \dots\dots\dots$ $Q_{calc} = \dots\dots\dots$

 $R_s = \dots\dots\dots$ $R_p = \dots\dots\dots$
 $R_{s \text{ theoretical}} = \dots\dots\dots$

$f=100kHz:$

$C_s = \dots\dots\dots$ $D = \dots\dots\dots$ $L = \dots\dots\dots$

Explanation:

6. Measuring the frequency-dependent behavior of a LC circuit

$L = \dots\dots\dots$ $C = \dots\dots\dots$

f(kHz)	1	5	10	12	15	18	20	50	100
L_e (measured)									
L_e (calculated)									
C_e (measured)									
C_e (calculated)									

Table 1

$f_{resonance} = \dots\dots\dots$

Explanation:

7. The study of an ohmmeter with Operational Amplifier

b) $R_{x1 \text{ measured}} = \dots\dots\dots$ $R_{x1 \text{ real}} = \dots\dots\dots$ $R_{x2 \text{ measured}} = \dots\dots\dots$ $R_{x2 \text{ real}} = \dots\dots\dots$

$\epsilon_{Rx1} [\%] = \dots\dots\dots$ $\epsilon_{Rx2} [\%] = \dots\dots\dots$

c) $R_{x3 \text{ measured}} = \dots\dots\dots$ $R_{x3 \text{ real}} = \dots\dots\dots$ $\epsilon_{Rx3} [\%] = \dots\dots\dots$

$R_{\text{potentiometer measured}} + R_{2 \text{ measured}} = \dots\dots\dots$ $V_{cc \text{ measured}} = \dots\dots\dots$ $R_{x \text{ CS}} = \dots\dots\dots$

d) Error sources and explanations: